



MONTCLAIR STATE
UNIVERSITY

Rana, Karan

Department of CSIT

Information Technology

FINAL PROJECT

Rana, Karan

CSIT230_SP21, 03

Instructor: Dr. G.E. Antoniou

Final Project

Problem 1

1.

Design a digital logic circuit (all steps are required), using minimal amount of gates, that will realize a digital logic circuit corresponding to the following *A097803 polynomial* :

$$A = 3(2x^2 + 1), \text{ with input } (x) : 0 \leq (x) \leq 7$$

(a) Set-up the truth-table

[Binary inputs: (x); Binary outputs: $A_1, A_2, A_3, A_4, \dots$]

	X1	X2	X3	A	A1	A2	A3	A4	A5	A6	A7	A8	A9
0	0	0	0	3	0	0	0	0	0	0	0	1	1
1	0	0	1	9	0	0	0	0	0	1	0	0	1
2	0	1	0	27	0	0	0	0	1	1	0	1	1
3	0	1	1	57	0	0	0	1	1	1	0	0	1
4	0	0	0	99	0	1	1	1	0	0	0	1	1
5	0	0	1	153	0	0	0	0	1	1	0	0	1
6	0	1	0	219	0	1	1	0	1	1	0	1	1
7	0	1	1	297	1	0	0	1	0	1	0	0	1

(b) Derive the output expressions

$$A1 = x1x2x3$$

$$A2 = x1x2'x3 + x1x2x3'$$

$$A3 = x1x2'x3' + x1x2x3'$$

$$A4 = x1'x2x3 + x1x2'x3' + x1x2x3$$

$$A5 = x1'x2x3' + x1'x2x3 + x1x2'x3 + x1x2x3'$$

$$A6 = x1'x2'x3 + x1'x2x3' + x1'x2x3 + x1x2'x3 + x1x2x3' + x1x2x3$$

$$A7 = 0$$

$$A8 = x1'x2'x3' + x1'x2x3' + x1x2'x3' + x1x2x3'$$

Final Project

(c) Simplify (optimally) the derived expressions, USING ONLY K-Maps

A1

	00	01	11	10
0	0	0	0	0
1	0	0	1	0

A2

	00	01	11	10
0	0	0	0	0
1	0	1	0	1

A3

	00	01	11	10
0	0	0	0	0
1	1	0	0	1

A4

	00	01	11	10
0	0	0	1	0
1	1	0	1	0

A5

Final Project

	00	01	11	10
0	0	0	1	1
1	0	1	0	1

A6

	00	01	11	10
0	0	1	1	1
1	0	1	1	1

A7

	00	01	11	10
0	0	0	0	0
1	0	0	0	0

A8


	00	01	11	10
0	1	0	0	1
1	1	0	0	1

A9

	00	01	11	10
0	1	1	1	1
1	1	1	1	1

Final Project

(d) Implement the simplified digital logic circuit, using *LogiSim*.

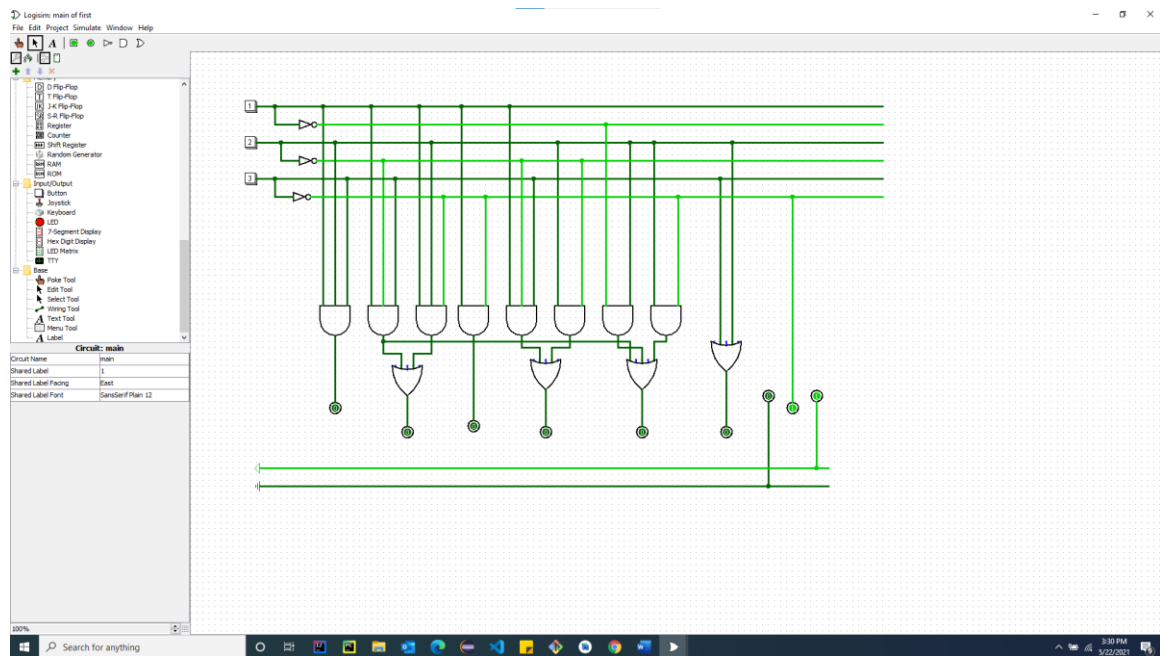

Problem 2

2. Design a Read Only Memory (ROM) to implement the following, *A097803*, polynomial

$$A = 3(2x^2 + 1), \text{ with input } (x) : 0 \leq (x) \leq 7$$

(a) What is the size of the initial (unsimplified) ROM ?

Knowing that it is a ROM we need 4-8 decoders and 16 or gates are needed.

(b) What is the size of the final (simplified) ROM ?

When the input $X = 0$

$$\rightarrow 3(2 \cdot (0)^2 + 1)$$

$$= 0$$

The same thing goes on when $X = 1, 2, 3, 4, 5, 6, 7, 8$

$$X = 1$$

Final Project

$$\begin{aligned} &= 3(2*(1)^2 + 1) \\ &= 9 \end{aligned}$$

$$\begin{aligned} X &= 2 \\ &= 3(2*(2)^2 + 1) \\ &= 27 \end{aligned}$$

$$\begin{aligned} X &= 3 \\ &= 3(2*(3)^2 + 1) \\ &= 57 \end{aligned}$$

$$\begin{aligned} X &= 4 \\ &= 3(2*(4)^2 + 1) \\ &= 99 \end{aligned}$$


$$\begin{aligned} X &= 5 \\ &= 3(2*(5)^2 + 1) \\ &= 153 \end{aligned}$$

$$\begin{aligned} X &= 6 \\ &= 3(2*(6)^2 + 1) \\ &= 219 \end{aligned}$$

$$\begin{aligned} X &= 7 \\ &= 3(2*(7)^2 + 1) \\ &= 297 \end{aligned}$$

(c) Show in detail the final ROM layout, using *LogiSim*.

Final Project

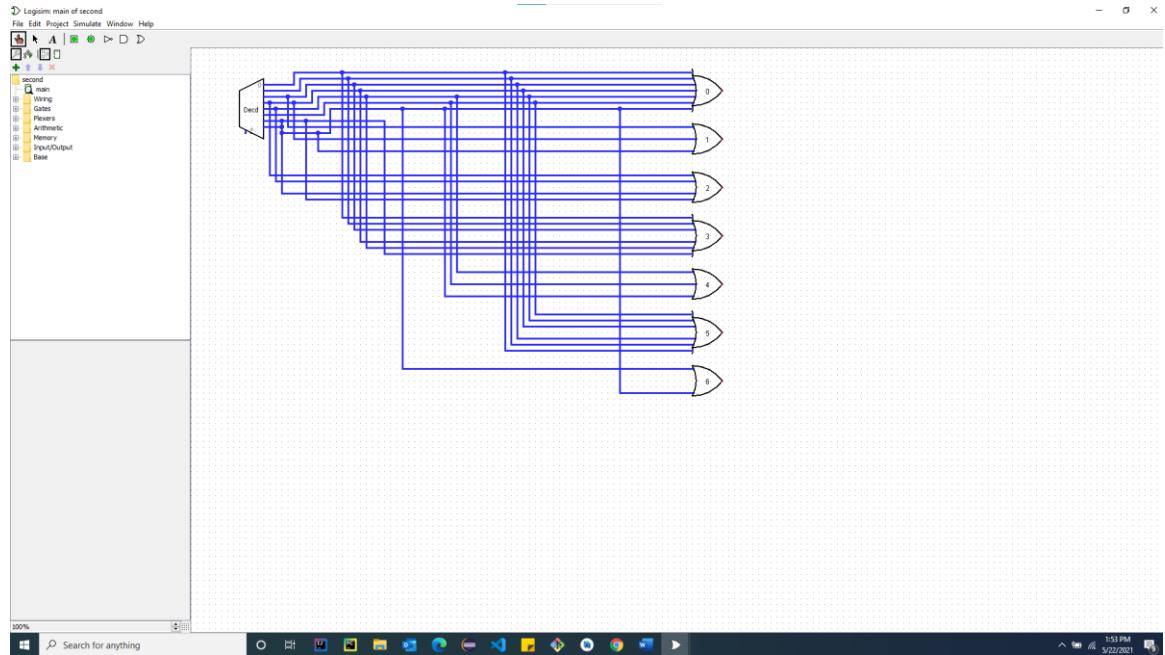

Problem 3

3.

Using MIPS assembly-language evaluate the following, *A097803*, polynomial:

$$A = 3(2x^2 + 1), \text{ for } x = 0, 1, 2, 3, 4, 5, 6, 7$$

- (a) The program should be simple modularized and well-documented
- (b) Appropriate comments in the program are necessary
- (c) Place the results, in the command line window (console). In the report include a clear screenshot of the DECIMAL results (command line window-console area) and the REGISTERS with the DECIMAL results

Final Project

(registers area)

(d) Indicate if the program runs successfully according to specifications and clearly state the results (DECIMAL numbers).

.data

```
pr1: .asciiz # formula A= 3(2*x^2+1)
newline: .asciiz#print new line
pr2: .asciiz #The Program run successfully
re1: .asciiz
```

.text

.globl main

main:

```
li $v0, 4 #call for string for 1
la $a0, pr1 #String being stored
syscall
```

```
li $v0, 4 # call for new line instructions
la $a0, newline # string being stored
syscall
```

```
li $t0, 0 #storing 0 in $t0
li $t1, 7 #storing 7 in $t1
```

startingloop:

```
mul $t2, $t0, $t0 #square root
mul $t2, $t2, 2 #multiplying 2 into t2
add $t2, $t2, 1 #adding 1 into t2
mul $t2, $t2, 3 #multiplying 3 into t2
li $v0, 4 #call for print string 1
la $a0, re1 #address of string
syscall
```


Final Project

```
li $v0, 1 #print new line integer
move $a0, $t2 #move t2 to a0
syscall
```

```
add $t0, $t0, 1 # 1++ incrementation
ble $t0,$t1,startingloop #loop
```

```
#finalloop
```

```
li $v0, 4 #call for new line
la $a0, newline #String loaded
syscall
```

```
li $v0, 4 #printing node 2
la $a0, pr2 #string location in register
syscall
```

```
li $v0, 10 #exit
syscall
```

