



Department of CSIT

Information Technology

Module 3

Rana, Karan


CSIT230_03SP

Problem 1

A heart rate monitor measures an individual's heart rate and blood pressure. Both sensors output zero (0) if they are within safety range. An alarm will sound if either sensor indicates an unsafe condition is present. Set-up the appropriate truth table, simplify (minimally) using K-maps. Implement, using Logisim, the simplified logic circuit with optimal number of logic gates.

X	Y
0	0
0	1
1	0
1	1

X or Y	0	1
0	0	1
1	1	1

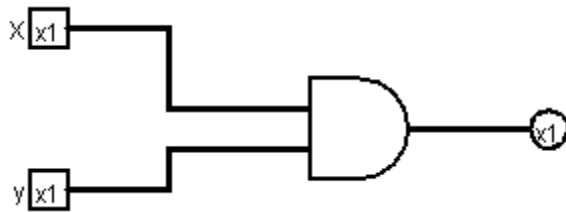

Problem 2

Three light-emitting diodes (LEDs) [one Red, one Green, one Blue] turn on when a number 0–7 is passed through. Red turns on with even numbers, green turns on with odd numbers, blue turns on with multiples of 3. Zero means they are all off, seven means they are all on. Set-up the appropriate truth table, simplify (minimally) using K-maps. Implement, using Logisim, the simplified logic circuit with optimal number of logic gates.


We know that even numbers turn on **Red** = 2,4,6

We know that odd numbers turn on **green** = 1,3,5

We know that blue numbers turn on **blue** = 3,6

Module 3

X/Y/Z	X	Y	Z
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

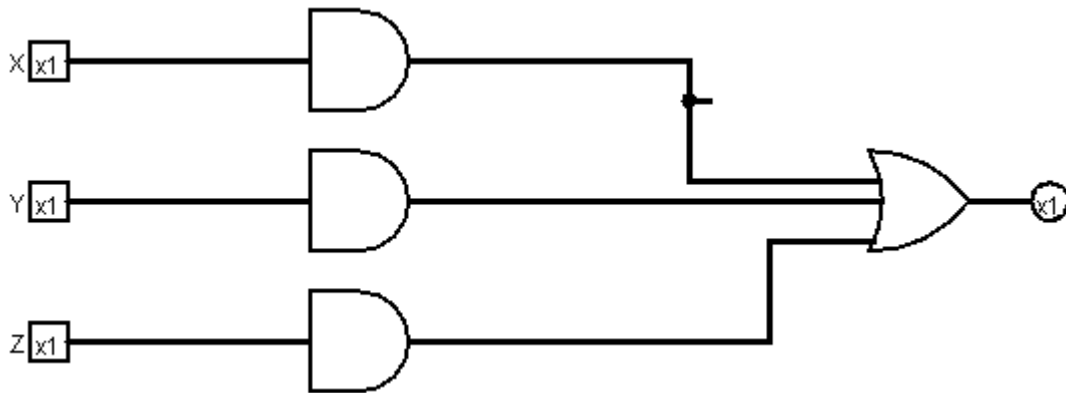


Problem 3

A teacher is grading the students in 4 subjects (Math, Spelling, English, and History) to see whether or not they will graduate. If a student passes Math and Spelling, they will graduate. If a student passes either English or History, they will graduate. All other students will not graduate. Set-up the appropriate truth table, simplify (minimally) using K-maps. Implement, using Logisim, the simplified logic circuit with optimal number of logic gates.

Math and Spelling = Graduate
 English or History = Graduate
 Rest = not graduate

Module 3

Math	Spelling	English	History	Graduate
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

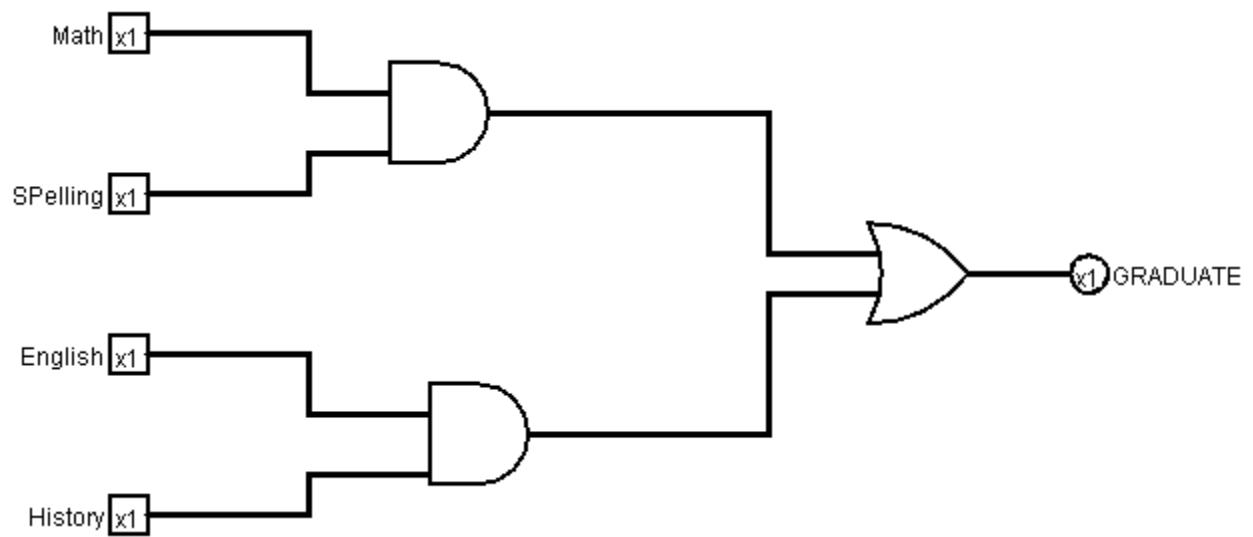

Problem 4

Design a digital logic circuit (LookUp Table or LUT) with three inputs, x, y and z, and the three outputs, A, B, and C. When the binary input is 0, 1, 2, or 3, the binary output is 2 greater than the input. When the binary input is 4, 5, 6, or 7, the binary output is 2 less than the input. Set-up the appropriate truth table, simplify (minimally) using K-maps. Implement, using Logisim, the simplified logic circuit with optimal number of logic gates.

X	Y	Z	A	B	C
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	0	1	1
1	1	0	1	0	0

1	1	1	1	0	1
---	---	---	---	---	---

